

College of Engineering, Pune  
Dept. of Electronics and Telecommunication Engineering

Course : RTL Simulation and Synthesis Lab (FY VLSI & ES)  
Year : 2020-21

RTL Lab 8 Report :

Mis : 122035014  
Name : Swapnil Hanmant Phalke

## RAM

```
module ram(clk,address, data,we,en,data_out
);
input clk,we,en;
input [4:0]address;
input [31:0]data;
reg [7:0]temp_data;
output [7:0]data_out;


reg [7:0]ram[31:0];

always@(posedge clk)
begin
if(we & en)
ram[address]=data;
end

always@(posedge clk)
begin
if(!we & en)
temp_data=ram[address];
end

assign data_out= en &!we ?temp_data : 'hz;

endmodule
```

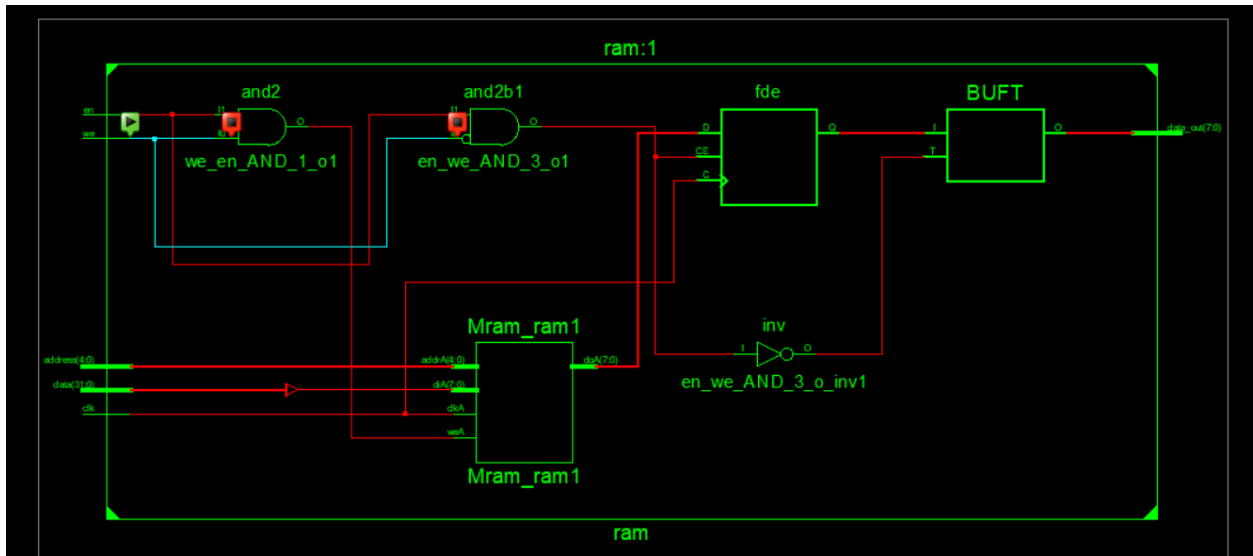

```
module ramtestbench;
```

```
    // Inputs
```

```
    reg clk;
```

```
    reg [4:0] address;
```

```
    reg [31:0] data;
```

```
    reg we;
```

```
    reg en;
```

```
    // Outputs
```

```
    wire [7:0] data_out;
```

```
    // Instantiate the Unit Under Test (UUT)
```

```
    ram uut (
```

```
        .clk(clk),
```

```
        .address(address),
```

```
        .data(data),
```

```
        .we(we),
```

```
        .en(en),
```

```
        .data_out(data_out)
```

```
    );
```

```

always
    #5 clk = ~clk;
integer i;
initial begin
    // Initialize Inputs


    clk = 1;
    we = 0;
    data = 0;
    address = 0;
    #20;
    //Write all the locations of RAM
    en = 1;
    we = 1;
    for(i=1; i <= 31; i = i + 1) begin
        data = i;
        address = i-1;
        #10;
    end
    en = 1;
    we = 0;
    //Read from port 1, all the locations of RAM.

    for( i=1; i <= 31; i = i + 1) begin
        address = i-1;
        #10;
    end

end

endmodule

```

 

## DualPort RAM

```
module dualport(clk1,din1,din2,cs,addr1,addr2,wen1,wen2,oen1,oen2,dout1,dout2);
```

```
    input cs,clk1,wen1,oen1,wen2,oen2;
```

```
    input [4:0] addr1;
```

```
    input [4:0] addr2;
```

```
    input [7:0] din1,din2;
```

```
    output [7:0] dout1,dout2;
```

```
    reg [7:0] temp_data1,temp_data2;
```

```
    reg [7:0] addr_ram1 [31:0];
```

```
    reg [7:0] addr_ram2 [31:0];
```

```
    always @ (posedge clk1)
```

```

begin
    if (clk1 & cs & wen1)
        addr_ram1[addr1] <= din1;
    end

    always @ (posedge clk1)
    begin
        if (clk1 & cs & wen2)
            addr_ram2[addr2] <= din2;
        end


        always @ (posedge clk1)
        begin
            if (clk1 & cs & !wen1)
                temp_data1 <= addr_ram1[addr1];
            end

            always @ (posedge clk1)
            begin
                if (clk1 & cs & !wen2)
                    temp_data2 <= addr_ram2[addr2];
                end

            assign dout1 = (cs & !wen1 & oen1) ? temp_data1 : 8'bzzzzzzzz;
            assign dout2 = (cs & !wen2 & oen2) ? temp_data2 : 8'bzzzzzzzz;

        Endmodule

```

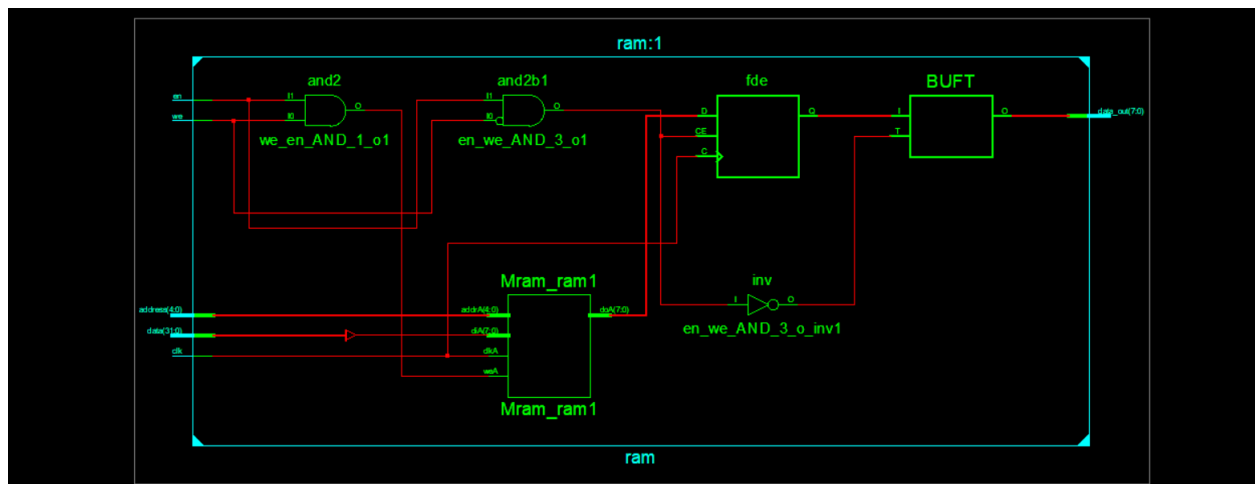

```
module dualport_ram_tb;
```

```
    // Inputs
```

```
    reg clk1;
```

```
    reg [7:0] din1;
```

```
    reg [7:0] din2;
```

```
    reg cs;
```

```
    reg [4:0] addr1;
```

```
    reg [4:0] addr2;
```

```
    reg wen1;
```

```
    reg wen2;
```

```
    reg oen1;
```

```
    reg oen2;
```

```
    // Outputs
```

```
    wire [7:0] dout1;
```

```
    wire [7:0] dout2;
```

```
    // Instantiate the Unit Under Test (UUT)
```

```
    dualport_ram_ uut (
```

```
        .clk1(clk1),
```

```
        .din1(din1),
```

```
        .din2(din2),
```

```
        .cs(cs),
```

```
        .addr1(addr1),
```

```
        .addr2(addr2),
```

```
        .wen1(wen1),
```

```
        .wen2(wen2),
```

```
        .oen1(oen1),
```

```
        .oen2(oen2),
```

```
        .dout1(dout1),
```

```
        .dout2(dout2)
```

```
    );
```

```
    initial begin
```

```
        clk1=1;
```

```
        forever clk1=#5 ~clk1;
```

```
    end
```

initial begin

// Initialize Inputs

din1 = 0;

din2 = 0;

cs = 0;

addr1 = 0;

addr2 = 0;

wen1 = 0;

wen2 = 0;

oen1 = 0;

oen2 = 0;

#50;

din1 = 8'b10101010;

din2 = 8'b00001111;

cs=1;

addr1 = 5'b00111;

addr2 = 5'b11000;

wen1 = 0;

wen2 = 1;

oen1 = 0;

oen2 = 0;

#50;

din1 = 8'b10101010;

din2 = 8'b01010100;

cs=1;

addr1 = 5'b00111;

addr2 = 5'b11000;

wen1 = 1;

wen2 = 0;

oen1 = 0;

oen2 = 1;

#50;

din1 = 8'b10101010;

din2 = 8'b01000010;

cs=1;


addr1 = 5'b00111;



```
addr2 = 5'b11000;  
wen1 = 0;  
wen2 = 0;  
oen1 = 1;  
oen2 = 0;  
#50;  
$finish;
```

```
end
```

```
endmodule
```

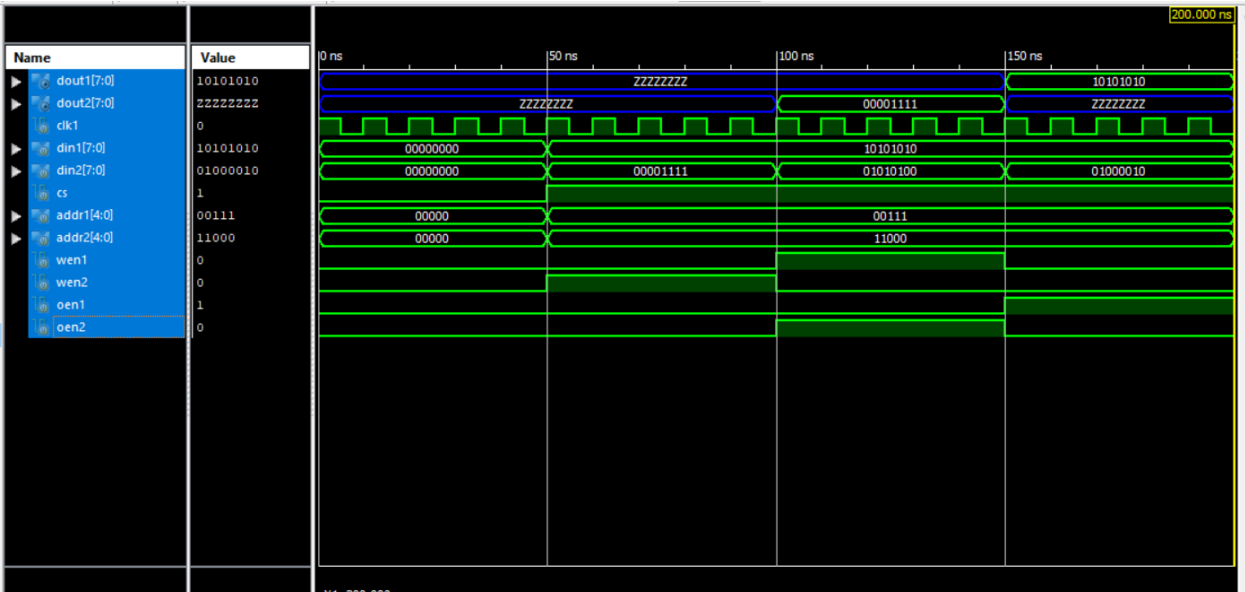

## FIFO

```
module FIFO_buffer(clk,datain,rd,wr,en,dataout,rst,empty,full
);
input clk,rd,wr,en,rst;
output empty,full;
input [31:0]datain;
output reg[31:0]dataout;
reg [2:0]count=0;
reg[31:0]FIFO[0:7];
reg [2:0]readcounter=0,
        writecounter=0;

assign empty=(count==0)?1'b1:1'b0;
assign full=(count==8)?1'b1:1'b0;
always@(posedge clk)
begin
    if(en==0);
    else
    if(rst)begin
        readcounter=0;
        writecounter=0;
    end

    else if(rd==1'b1 && count!=0)begin
        dataout=FIFO[readcounter];
```

```


        readcounter=readcounter+1;
    end

    else if(wr==1'b1 && count<8) begin
        FIFO[writecounter]=datain;
        writecounter=writecounter+1;
    end
end
else if(writecounter==8)begin
    writecounter=0;
end
else if(readcounter==8)begin
    readcounter=0;
end
else if(readcounter>writecounter)begin
    count=readcounter-writecounter;
end
else if(writecounter>readcounter)begin
    count=writecounter-readcounter;
end

end

end
Endmodule

```

 

```

module FIFO_test;

    // Inputs
    reg clk;
    reg [31:0] datain;
    reg rd;
    reg wr;
    reg en;
    reg rst;

    // Outputs
    wire [31:0] dataout;
    wire empty;
    wire full;

    // Instantiate the Unit Under Test (UUT)
    FIFO_buffer uut (
        .clk(clk),
        .datain(datain),
        .rd(rd),
        .wr(wr),
        .en(en),
        .dataout(dataout),
        .rst(rst),
        .empty(empty),
        .full(full)
    );

    initial begin
        // Initialize Inputs
        clk = 0'b0;
        datain = 32'h0;
        rd = 1'b0;
        wr = 1'b0;
        en = 1'b0;
        rst = 1'b1;

        // Wait 100 ns for global reset to finish
        #100;
    end
endmodule

```


```
    en = 1'b1;
    rst = 1'b1;

    // Wait 100 ns for global reset to finish
    #20;

    rst=1'b0;
    wr=1'b1;
    datain=32'h0;
    #20;

    datain=32'h0;
    #20;
    datain=32'h1;
    #20;
    datain=32'h2;
    #20;
    datain=32'h3;
    #20;
    datain=32'h4;
    #20;
    wr=1'b0;
    rd=1'b1;

    end
    always#10clk=~clk;
Endmodule
```

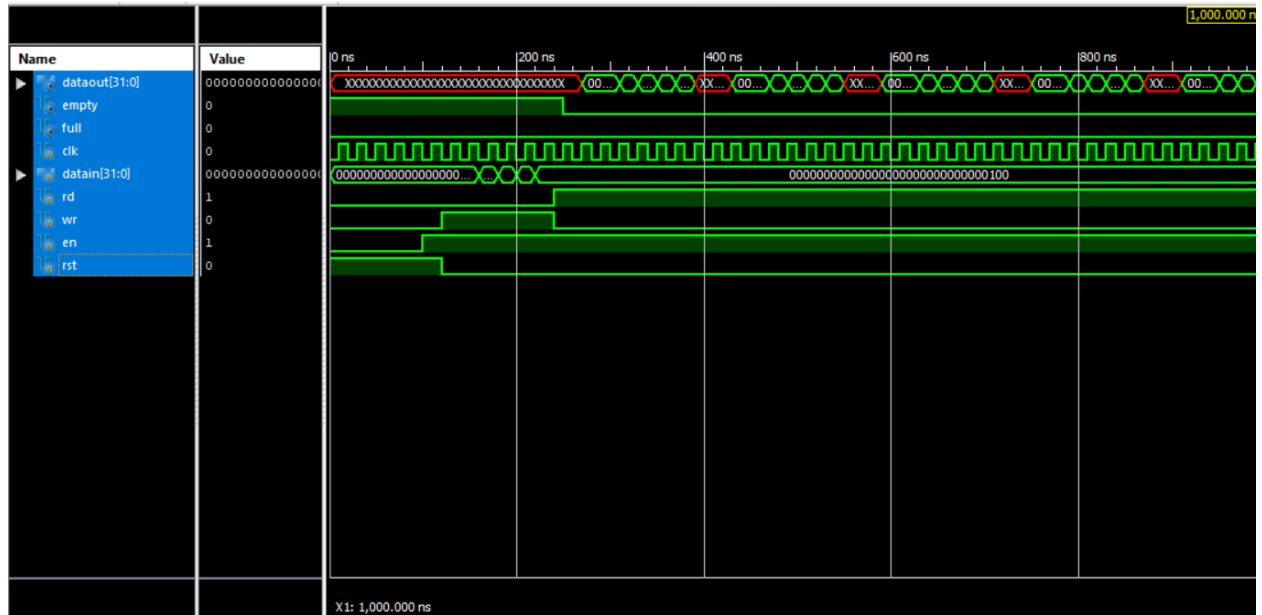

## Serial Adder

```
module shift(y,d,clk);
input [3:0] d;
input clk;
output [3:0] y;
reg [3:0] y;
```

```
always @(posedge clk)
begin
y[0]=d[1];
y[1]=d[2];
y[2]=d[3];
y[3]=1'b0;
end
endmodule
```

//serial in parallel out register to store the 4 bit sum

```
module sipo(y,s,clk);
input s;
input clk;
```

```

output [3:0] y;
reg [3:0] y;
always @(posedge clk)
begin
y={s,y[3:1]};
end
endmodule

```

```

//1 bit full adder
module fa(s,cout,a,b,cin);
input a,b,cin;
output s,cout;
assign s=a^b^cin;
assign cout=a&b|b%cin|cin&a;
endmodule

```

```

//d flipflop to store the cout of each stage
module dff(q,d,clk);
input d,clk;
output q;
reg q;
initial begin
q=1'b0;
end
always @(posedge clk)
begin
q=d;
end
endmodule

```

```

//main module serial adder//
module serial(sum,cout,a,b,clk);
input [3:0] a,b;
input clk;
wire [3:0] x,z;
output [3:0] sum;
output cout;
wire s,cin;
//input cin;
//initial begin

```

```

//cin=cinp;
//end
fa k(s,cout,x[0],z[0],cin);      //1 bit full adder
dff q(cin,cout,clk);             //d flipflop to store the cout value after each 1 bit full
addder operation

sipo m(sum,s,clk);               //serial sum(s) converted to parallel output(4 bit sum)///

shift g(x,a,clk);                //shifts the input a
shift h(z,b,clk);                //shifts the input b
endmodule

```



