

# College of Engineering, Pune


Dept. of Electronics and Telecommunication Engineering

---

Course : **RTL Simulation and Synthesis Lab (FY VLSI & ES)**

Year : 2020-21

---

 

## RTL Lab 1,2,3 Report :

**Mis : 122035014**

**Name : Phalke Swapnil Hanmant**

## Question1:Half Adder

module halfadd( a,b,sum,carry);


input a,b;

output sum,carry;

assign sum=a^b;

assign carry=a&b;

endmodule

 


## Question 2:

1. Draw TT and simplify using k-maps if a 4 input function has conditions that output is high if inputs has exactly 2 zeros or exactly 2 ones or exactly 3 ones

- Behavioural

```
module problem1_0(a,b,c,d,out);
input a,b,c,d;
output reg out;
reg [3:0]q;
```

```
always@(*)
begin
q[0]=a;
q[1]=b;
q[2]=c;
q[3]=d;
case(q)
4'b0000 : out = 0;
4'b0001 : out = 0;
4'b0010 : out = 0;
4'b0011 : out = 1;
4'b0100 : out = 0;
4'b0101 : out = 1;
4'b0110 : out = 1;
4'b0111 : out = 1;
4'b1000 : out = 0;
4'b1001 : out = 1;
4'b1010 : out = 1;
4'b1011 : out = 1;
4'b1100 : out = 1;
4'b1101 : out = 1;
4'b1110 : out = 1;
4'b1111 : out = 0;
default: out = 0;
endcase
end
endmodule
```

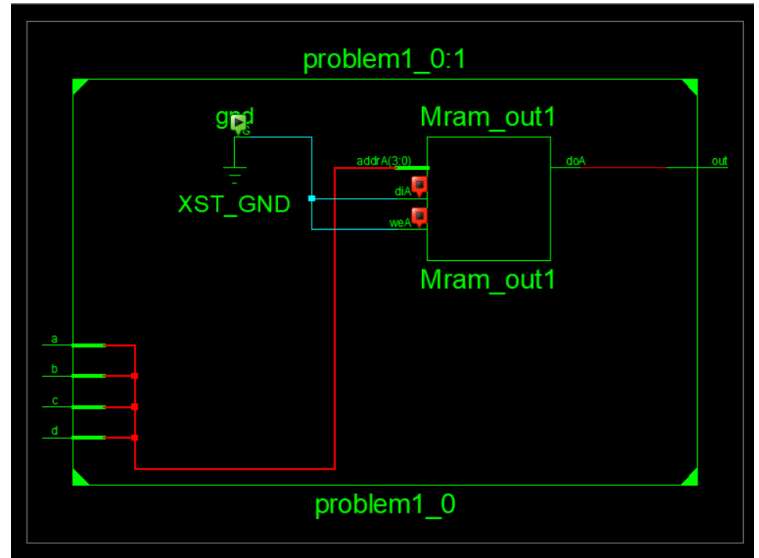

## Testbench Code and Simulation

### Result:

```
module test;
// Inputs
reg a;
reg b;
reg c;
reg d;
// Outputs
wire out;
// Instantiate the Unit Under Test (UUT)
problem1_0 uut (
.a(a), .b(b), .c(c), .d(d), .out(out));
initial begin
a = 0;
b = 0;
c = 0;
d = 0;
#100;
a = 0;b = 0;c = 0;d = 1;
#100;
a = 0;b = 0;c = 1;d = 0;
#100;
a = 0;b = 0;c = 1;d = 1;
#100;
a = 0;b = 1;c = 0;d = 0;
#100;
a = 0;b = 1;c = 0;d = 1;
#100;
a = 0;b = 1;c = 1;d = 0;
#100;
a = 0;b = 1;c = 1;d = 1;
end
endmodule
```




- **Structural**

```

module problem1_1(
    a,b,c,d,out);
    input a,b,c,d;
    output out;
    wire q,w,e,r;
    wire a1,a2,a3,a4,a5,a6;
    not(q,a);
    not(w,b);
    not(e,c);
    not(r,d);
    and(a1,c,d,q);
    and(a2,b,d,q);
    and(a3,b,c,r);
    and(a4,a,d,w);
    and(a5,a,w,c);
    and(a6,a,b,e);
    or(out,a1,a2,a3,a4,a5,a6);
endmodule

```

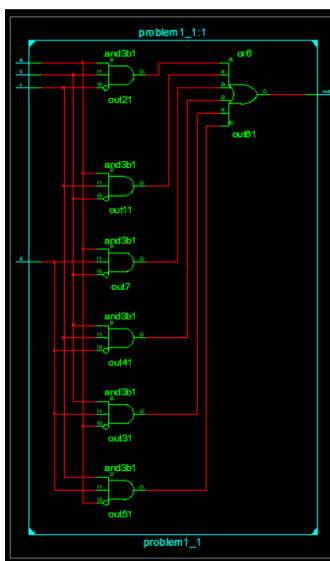

### Testbench Code and Simulation Result:

```

module tesst;
// Inputs
    reg a;
    reg b;
    reg c;


```

```

    reg d;
    // Outputs
    wire out;
    // Instantiate the Unit Under Test (UUT)
    problem1_1 uut (
        .a(a),
        .b(b),
        .c(c),
        .d(d),
        .out(out)
    );
    initial begin
        // Initialize Inputs
        a = 0;
        b = 0;
        c = 0;
        d = 0;

        #100;
        a = 0;b = 0;c = 0;d = 1;
        #100;
        a = 0;b = 0;c = 1;d = 0;
        #100;
        a = 0;b = 0;c = 1;d = 1;
        #100;
        a = 0;b = 1;c = 0;d = 0;
        #100;
        a = 0;b = 1;c = 0;d = 1;
        #100;
        a = 0;b = 1;c = 1;d = 0;
        #100;
        a = 0;b = 1;c = 1;d = 1;
        end
endmodule

```

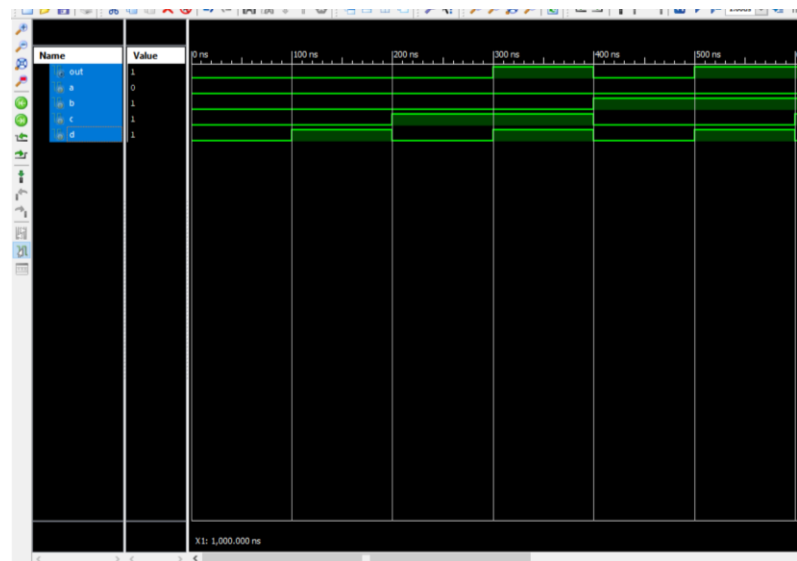

2. In a factory, if relay A is ON then indicator glows except condition that if both B and C are ON, and if A is OFF then indicator glows only when relay D is ON. Find the TT and simplify using k-map.

- **Behavioral**

```

module problem2_0(a,b,c,d,out);
    input a,b,c,d;
    output reg out;
    reg [3:0]q;

```

The screenshot displays a Verilog HDL code editor with a circuit diagram for 'problem2\_0'. The diagram features a memory block labeled 'Mram\_out1' with inputs 'addrA(3,0)', 'dIA', and 'weA', and an output 'doA'. A ground symbol is connected to 'XST\_GND'. A bus 'a' is shown with signals 'b', 'c', and 'd'.

```

module tesst;
// Inputs
    reg a;
    reg b;
    reg c;
    reg d;
// Outputs
    wire out;

// Instantiate the Unit Under Test (UUT)
    Problem2_0 uut (
        .a(a),
        .b(b),
        .c(c),
        .d(d),
        .out(out)
    );

    initial begin
        // Initialize Inputs

```

```

a = 0;
b = 0;
c = 0;
d = 0;

#100;
a = 0;b = 0;c = 0;d = 1;

#100;
a = 0;b = 0;c = 1;d = 0;

#100;
a = 0;b = 0;c = 1;d = 1;


#100;
a = 0;b = 1;c = 0;d = 0;

#100;
a = 0;b = 1;c = 0;d = 1;

#100;
a = 0;b = 1;c = 1;d = 0;

#100;
a = 0;b = 1;c = 1;d = 1;
end
endmodule

```

 

- **Structural**

```


module problem2_1(
    a,b,c,d,out);

    input a,b,c,d;
    output out;
    wire q,w,e,r;
    wire a1,a2,a3;

    not(q,a);
    not(w,b);
    not(e,c);
    not(r,d);
    and(a1,q,d);
    and(a2,a,w);
    and(a3,a,e);
    or(out,a1,a2,a3);

```

endmodule

 


#### Testbench Code and Simulation Result:

```

module tesst;
// Inputs
    reg a;
    reg b;
    reg c;
    reg d;
// Outputs
    wire out;
// Instantiate the Unit Under Test (UUT)
    Problem2_1 uut (
        .a(a),
        .b(b),
        .c(c),
        .d(d),
        .out(out)
    );
    initial begin
        // Initialize Inputs
        a = 0;
        b = 0;
        c = 0;
        d = 0;

        #100;
        a = 0;b = 0;c = 0;d = 1;
        #100;
        a = 0;b = 0;c = 1;d = 0;
        #100;
        a = 0;b = 0;c = 1;d = 1;
        #100;
        a = 0;b = 1;c = 0;d = 0;
        #100;
        a = 0;b = 1;c = 0;d = 1;
        #100;
        a = 0;b = 1;c = 1;d = 0;
        #100;
        a = 0;b = 1;c = 1;d = 1;
    end
endmodule

```

 


#### Half adder

```

module half_add(
    input a,b,
    output sum,carry
);

    xor(sum,a,b);
    and(carry,a,b);
Endmodule

```

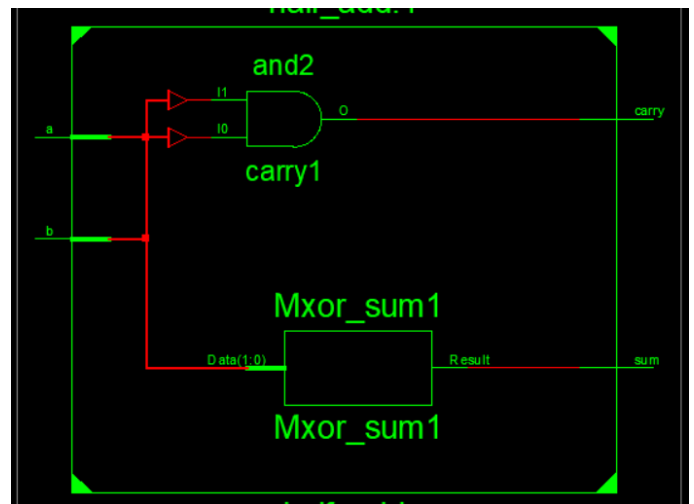

#### Testbench Code and Simulation Result:

```

module half_add_tb;
// Inputs
    reg a;
    reg b;

// Outputs
    wire sum;
    wire carry;

// Instantiate the Unit Under Test (UUT)


```

```

half_add uut (
    .a(a),
    .b(b),
    .sum(sum),
    .carry(carry)
);
initial begin
    // Initialize Inputs
    a = 0;
    b = 0;
    // Wait 100 ns for global
reset to finish
    #100;
    a=0;
    b=1;
    #100
    a=1;
    b=1;

end
endmodule


```

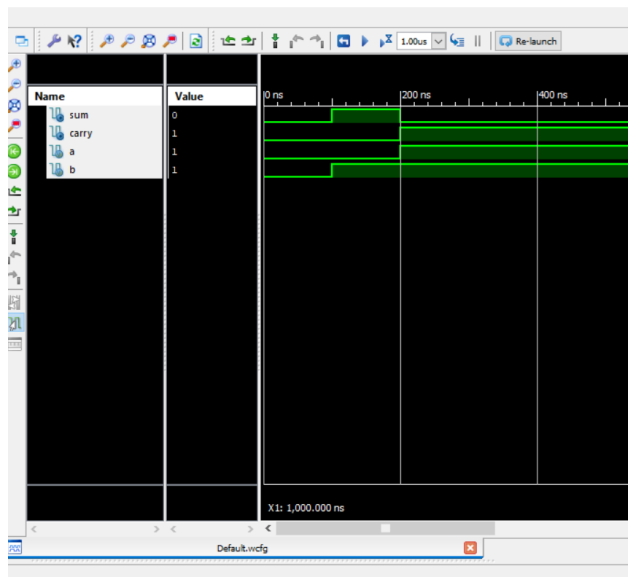


#### Question4:FA using HA

```
module FA( a,b,cin,sum
    );
input a,b,cin;
output cout,sum;
wire x,v,z;
HalfAdder h1(a,b,x,v);
HalfAdder h2(x,cin,sum,z);
assign cout=v|z;
endmodule
```
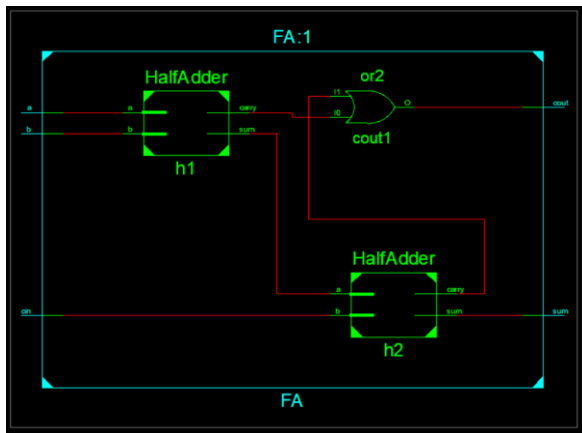
```
module HalfAdder( a,b,sum,carry
    );
input a,b;
output sum,carry;
assign sum=a^b;
assign carry=a&b;
endmodule
```


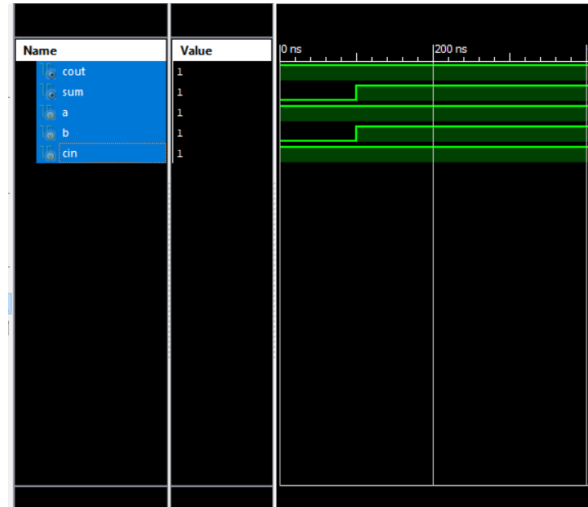
```
initial begin
a = 1;
    b = 0;
    cin = 1;
#100;
    a = 1;
    b = 1;
    cin = 1;
#100;
end
```





#### Question 5:4 bit ripple carry adder

```

module adder_4bit( a,b,sum,cin,cout
    );
input[0:3] a,b;
input cin;
output [0:3]sum;
output cout;
wire [1:3]x;

fulladd f1(a[0],b[0],cin,x[1],sum[0]);
fulladd f2(a[1],b[1],x[1],x[2],sum[1]);
fulladd f3(a[2],b[2],x[2],x[3],sum[2]);
fulladd f4(a[3],b[3],x[3],cout,sum[3]);
endmodule

```


```

module fulladd( a,b,cin,cout,sum
    );
input a,b,cin;
output cout,sum;

assign sum=a^b^cin;
assign cout=(a&b)|(b&cin)|(a&cin);

endmodule

```

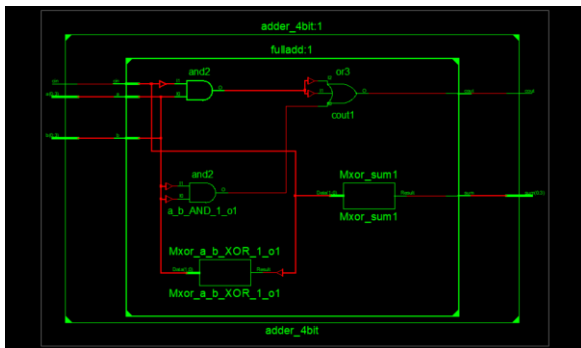

initial begin

// Initialize Inputs

```

a = 0;
b = 0;
cin = 0;
#100;
a = 1;
b = 0;
cin = 1;
#100;
a = 1;
b = 1;
cin = 1;

```

end




### Question 6: 8:1 using 4:1 and 2:1

```
module mux816(in.sel.out
_);
input [0:7]in;
input [0:2]sel;
output out;
wire x,y;
mux416 m1(in[0].in[1].in[2].in[3].sel[1:2].x);
mux416 m2(in[0].in[1].in[2].in[3].sel[1:2].y);
mux216 m3(x.y.sel[0].oit);
endmodule
```


```
module mux416(a.b.c.d.sel.out
_);
input a.b.c.d;
input [0:1]sel;
output out;
assign out=(~sel[0] & ~sel[1]&a) | (~sel[0] & sel[1]&b)
| (sel[0] & ~sel[1]&c) | (sel[0] & sel[1]&d);
endmodule
```

```
module mux216(a.b.sel.out
_);
input a.b;
input sel;
output out;
reg x,y;
assign out=(~sel &a) | (sel &b);
endmodule
```

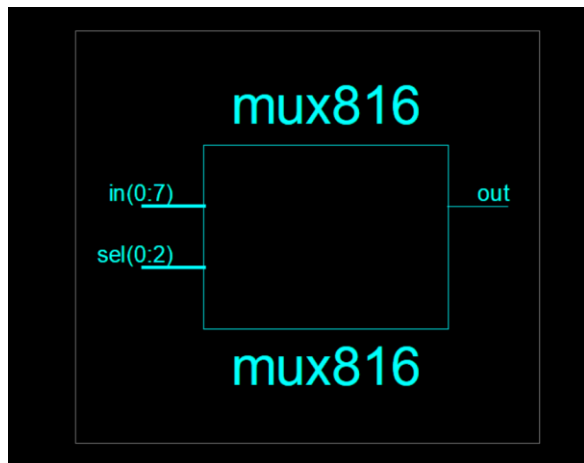

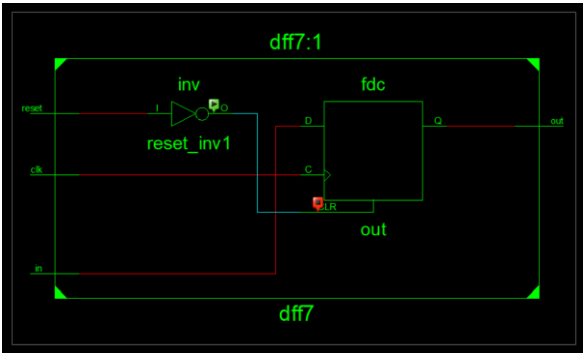**Question7: Dff using asynchronous reset**

```
module dff7( in,clk,reset,out
__);
input in,clk,reset;
output reg out;
always@(posedge clk, negedge reset)
begin
if(!reset)
out=0;
else
out=in;
end
endmodule
```



```
initial begin
// Initialize Inputs
in = 0;
clk = 0;
reset = 0;

// Wait 100 ns for global reset to
finish
#100;
in = 1;
clk = 1;
reset = 1;
// Add stimulus here
#100;
in = 1;

clk = 1;
reset = 0;

end
```



### Question 8: TFF using DFF

```
module Tflip(t.out,clk,rst,qbar):
```

```
input t.clk,rst;
```

```
output out,qbar;
```

```
wire o,p;
```

```
assign o=out;
```

```
assign p=t^o;
```

```
dflip d(p,rst,clk,out);
```

```
assign qbar=~out;
```

```
endmodule
```

```
module dflip(
```

```
    d,rst,clk,q);
```

```
input d,rst,clk;
```

```
output reg q;
```

```
always@(negedge clk or posedge rst )
```

```
begin
```

```
if(rst)
```


```
q=1'b0;
```

```
else
```

```
q=d;
```


```
end
```

```
endmodule
```

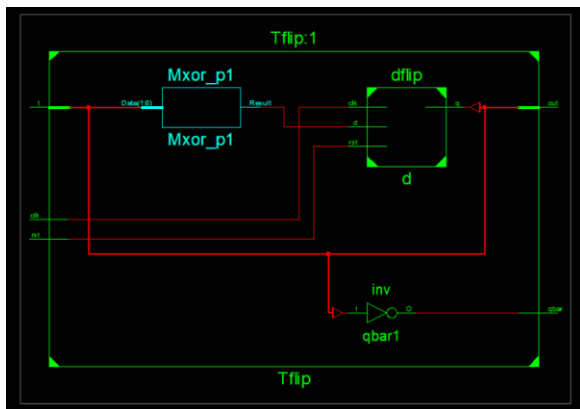
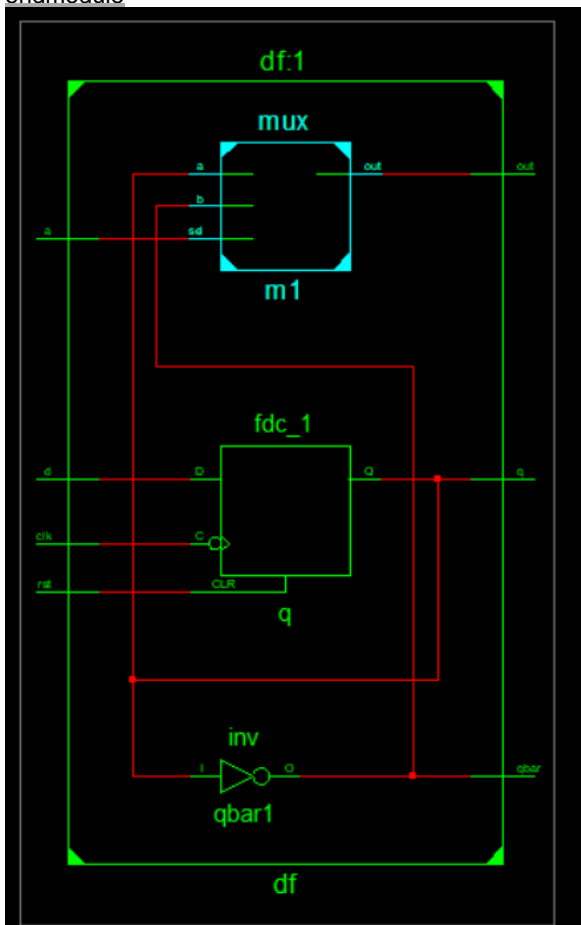
### Question9: Dff+Mux

```
module df(  
    d,rst,clk,q,a,qbar,out);  
input d,rst,clk,q,a,qbar,out;  
output reg q;  
output out;  
output qbar;  
always@(negedge clk or posedge rst )  
begin  
if(rst)  
q=1'b0;  
else  
q=d;  
end  
assign qbar=~q;  
mux m1(q,qbar,a,out);  
endmodule
```



### Question 10: 3bit counter using TFF

```
module threebit(q1,q2,q3,q1bar,q2bar,q3bar,clk,rst  
_);
```

```
input clk,rst;
```


```
output q1,q2,q3,q1bar,q2bar,q3bar;
```

```
Tflip t1(1'b1,q1,clk,rst,q1bar);
```

```
Tflip t2(1'b1,q2,q1bar,rst,q2bar);
```

```
Tflip t3(1'b1,q3,q2bar,rst,q3bar);
```

```
endmodule
```

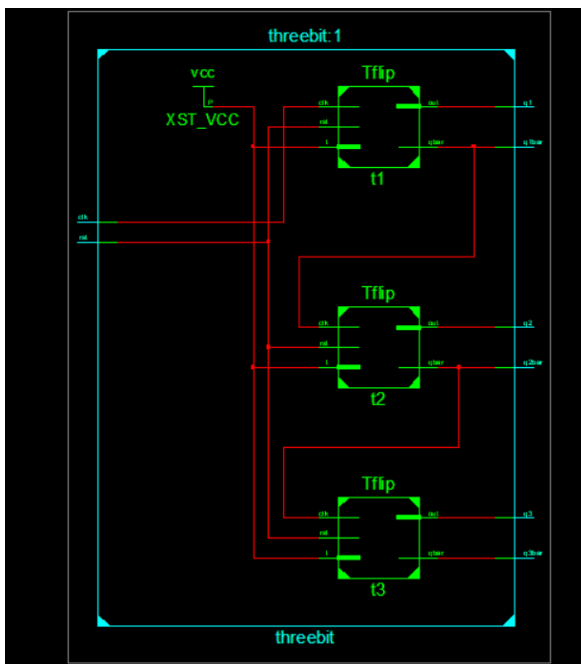

### Question 16: TFF using behavioral logic

```
module Tflipflop(t,out,clk,rst,qbar);
```

```
input t,clk,rst;
```

```
output reg out;
```

```
output qbar;
```

```
always@(negedge clk or posedge rst )
```

```
begin
```

```
if(rst)
```

```
out=0;
```

```
else if(t==0)
```

```
out=out;
```


```
else
```

```
out=~out;
```

```
end
```


```
assign qbar=~out;
```

```
endmodule
```

 

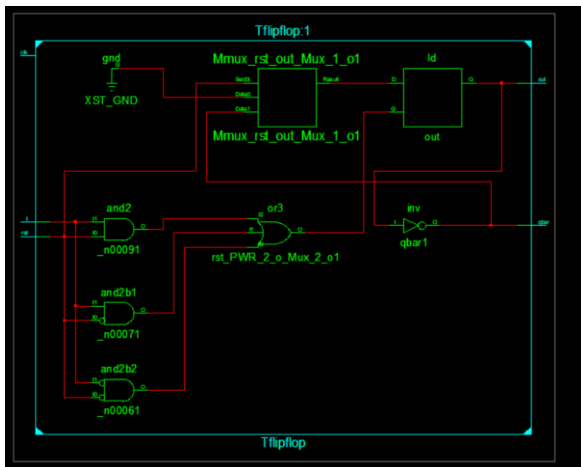
### Question 17: TFF using case logic

```
module Tflipflop(t.clk.rst.qbar):  
input t.clk.rst:  
output reg out:  
output qbar:  
always@(negedge clk or posedge rst )  
begin  
case({rst,t})  
2'b00 : out=0;  
2'b01 : out=0;  
2'b10 : out=out;  
2'b11 : out=~out;  
endcase  
end  
assign qbar=~out;  
endmodule
```


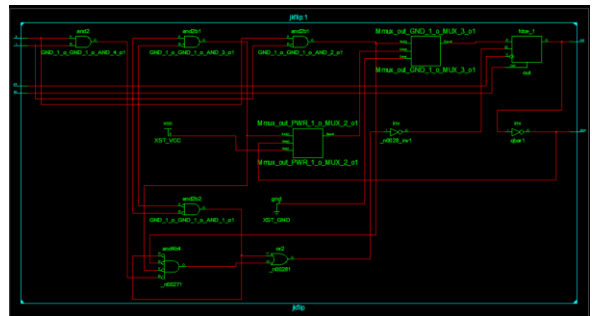
### Question18: JK using if else

```
module jkflip(j.k.out.clk.rst.qbar):  
input j.k.clk.rst:  
output reg out:  
output qbar:  
always@(negedge clk or posedge rst )  
begin  
if(rst)  
out=0;  
else if(i==0 && k==0)  
out=out;  
else if(i==0 && k==1)  
out=0;  
else if(i==1 && k==0)  
out=1;  
else if(i==1 && k==1)  
out=~out;  
end  
assign qbar=~out;  
endmodule
```





### Question 11-12 6bit up down

```
module updown6(  
  Clk,  
  reset,  
  UpOrDown, //high for UP counter and low for Down  
  counter  
  Count  
);  
//input ports and their sizes  
input Clk,reset,UpOrDown;  
//output ports and their size  
output [5 : 0] Count;  
//Internal variables  
reg [5 : 0] Count = 0;  
always @(posedge(Clk) or posedge(reset))  
begin  
  if(reset == 1)  
    Count <= 0;  
  else  
    if(UpOrDown == 1) //Up mode selected  
      if(Count == 15)  
        Count <= 0;  
      else  
        Count <= Count + 1; //Increment Counter  
    else //Down mode selected  
      if(Count == 0)  
        Count <= 15;  
      else  
        Count <= Count - 1; //Decrement counter  
  end  
end  
endmodule
```

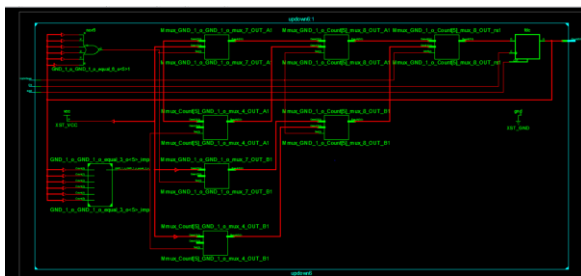 
### Question14: 6 bit shift register

```
module updown6 (C, SI, SO):  
  input C,SI:  
  output SO:  
  reg [5:0] tmp:  
  =  
  always @(posedge C)  
  begin  
    tmp = tmp << 1;  
    tmp[0] = SI;  
  end  
  assign SO = tmp[5];  
endmodule
```




 
### Question3: 4:1 MUX with 5 different coding Styles



```

module mux_4to1(a,b,c,d,sel,out,in
__);
input [0:3]in;
input a,b,c,d;
input [0:1]sel;
output [0:4]out;
reg x,y;
assign out[0]=(~sel[0] & ~sel[1]&a) | (~sel[0] &
sel[1]&b) | (sel[0] & ~sel[1]&c) | (sel[0] &
sel[1]&d);
always@(*)
begin
case(sel)
2'b00 : v=a;
2'b01 : v=b;
2'b10 : v=c;
2'b11 : v=d;
endcase
end
assign out[1]=v;
assign out[2] = sel[1] ? (sel[0] ? b : a ) : (sel[0] ?
d : c );
assign out[3]=in[sel];
wire NS0, NS1;
wire Y0, Y1, Y2, Y3;
not N1(NS0, sel[0]);
not N2(NS1, sel[1]);
and A1(Y0, a, NS1, NS0);
and A2(Y1, b, NS1, sel[0]);
and A3(Y2, c, sel[1], NS0);
and A4(Y3, d, sel[1], sel[0]);
or O1(out[4], Y0, Y1, Y2, Y3);
endmodule

```