

College of Engineering, Pune
Dept. of Electronics and Telecommunication Engineering

Course : RTL Simulation and Synthesis Lab (FY VLSI & ES)
Year : 2020-21

RTL Lab 6,7 Report :

Mis : 122035014
Name : Swapnil Hanmant Phalke

VENDING MACHINE

```
module vending( clk, reset, coin, vend, change
);
input clk, reset;
input wire[2:0] coin;

output reg vend;
output reg [2:0] change;

reg [2:0] y, Y;

parameter idle = 3'b000,
            five = 3'b001,
            ten = 3'b010,
            fifteen = 3'b011,
            twenty = 3'b100,
            twentyfive = 3'b101;

parameter nickel=3'b001,
            dime=3'b010,
            nickeldime=3'b011,
            dimedime=3'b100,
            quarter=3'b101;

always @ (posedge clk or negedge reset)
begin
    if (!reset)
        y <= idle;
    else
        y <= Y;
end

always @ (y, coin)
begin
    case (y)

        idle: case (coin)
            nickel: Y <= five;
            dime: Y <= ten;
            quarter: Y <= twentyfive;
            default: Y <= idle;
        endcase
    endcase
end
```

```
five: case (coin)
    nickel: Y <= ten;
    dime:    Y <= twenty;
    quarter: Y <= twentyfive;
    default: Y <= five;
endcase
```

```
ten: case (coin)
    nickel: Y <= fifteen;
    dime:    Y <= twenty;
    quarter: Y <= twentyfive;
    default: Y <= ten;
endcase
```

```
fifteen: case (coin)
    nickel: Y <= twenty;
    dime:    Y <= twentyfive;
    quarter: Y <= twentyfive;
    default: Y <= fifteen;
endcase
```

```
twenty: case (coin)
    nickel: Y <= twentyfive;
    dime:    Y <= twentyfive;
    quarter: Y <= twentyfive;
    default: Y <= twenty;
endcase
```

```
twentyfive: Y <= idle;
```

```
default: Y <= idle;
endcase
end
```

```
always @ (posedge clk or negedge reset)
begin
    if (!reset) begin
        vend <= 0;
        change <= 3'b000;
```

end

else case (y)

```
idle: begin
vend <= 0;
change <= 3'b000;
end
```

```
five: begin
vend <= 0;
if (coin == quarter)
change <= nickel;
else
change <= 3'b000;
end
```

```
ten: begin
vend <= 0;
if (coin == quarter)
change <= dime;
else
change <= 3'b000;
end
```

```
fifteen: begin
vend <= 0;
if (coin == quarter)
change <= nickeldime;
else
change <= 3'b000;
end
```

```
twenty: begin
vend <= 0;
if (coin == dime)
change <= nickel;
else if (coin == quarter)
change <= dimedime;
else
change <= 3'b000;
end
```

twentyfive: begin

```

vend <= 1;
change <= 3'b000;
end

```

```

default: begin
vend <= 0;
change <= 3'b000;
end

```

```


endcase

```

```

end
endmodule

```

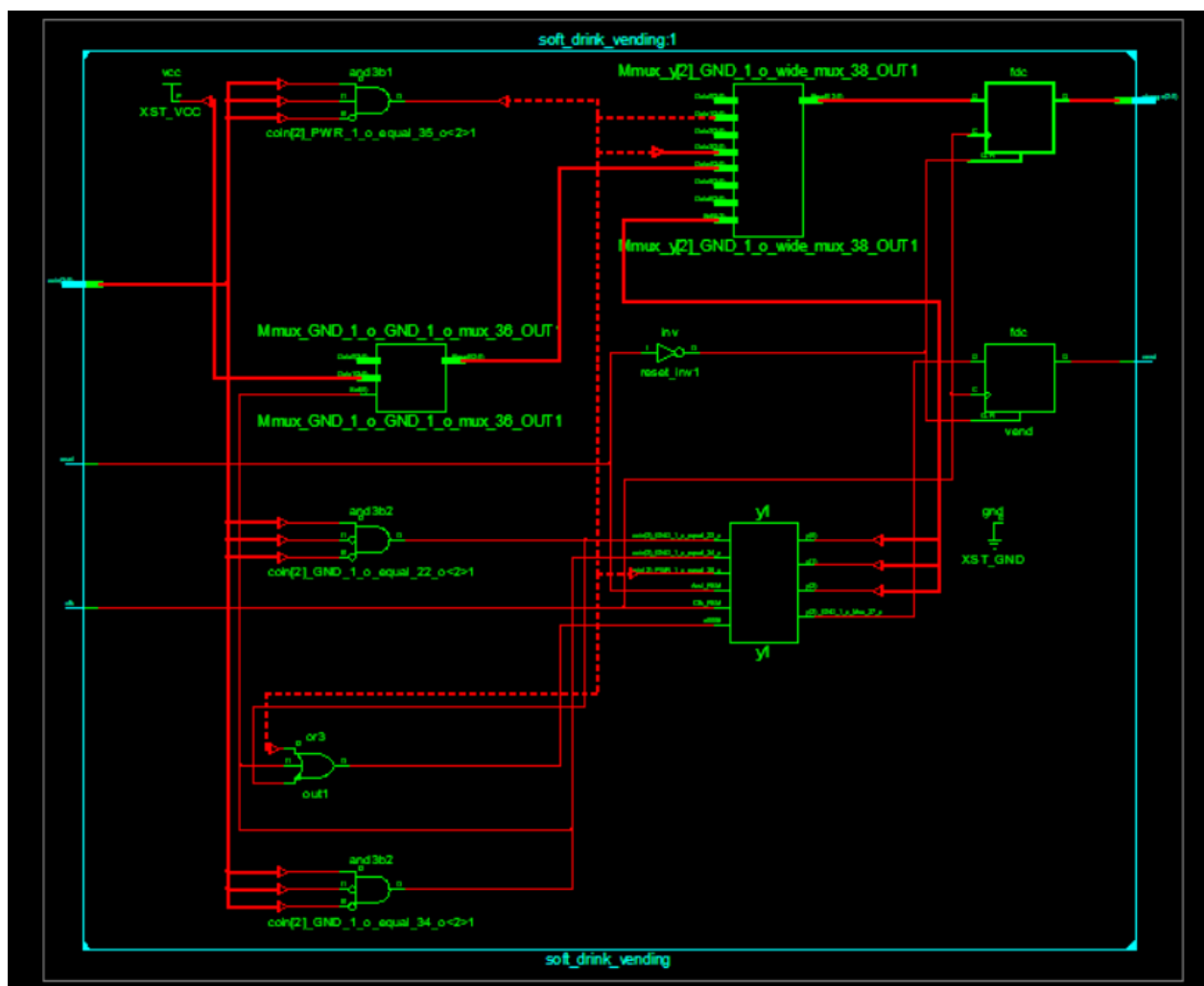

```

module Vending_test;

```

```

// Inputs

```

```

reg clk;
reg reset;
reg [2:0] coin;

// Outputs
wire vend;
wire [2:0] change;

// Instantiate the Unit Under Test (UUT)
soft_drink_vending uut (
    .clk(clk),
    .reset(reset),
    .coin(coin),
    .vend(vend),
    .change(change)
);

initial begin
    clk = 1;
    forever #5 clk = ~clk;
end

initial begin
    // Initialize Inputs

    reset = 0;
    #100;
    reset = 1;
    repeat(5)
    begin
        coin = $random;
        #100;
    end


    // Wait 100 ns for global reset to finish
    #100;

    // Add stimulus here

end

endmodule

```

 

Washing Machine

```


module wash(out, clk,lid,coin,cancel,mode1, rst);
output out;
input rst;
input clk,lid,coin,cancel,mode1;
reg coin_rtrn,out;
reg[5:0] state;
parameter idle=3'd0, ready=3'd1, soak=3'd2, wash=3'd3,rinse=3'd4,spin=3'd5;
always @(posedge clk or negedge rst)
if(rst==0) begin state=idle; out=0; end
else begin
case (state)
idle: begin out=0; if(cancel==0 && lid==0 && coin==1) state=ready; else state=idle; end
ready: begin out=0; if(cancel==0 && lid==0 && mode1==1) state=soak; else if(cancel==1)
state=idle; else state=ready; end
soak: begin out=0; if(cancel==0 && lid==0 && mode1==1) state=wash; else if(cancel==1)
state=idle; else state=soak; end
wash: begin out=0; if(cancel==0 && lid==0 && mode1==1) state=rinse; else if(cancel==1)
state=idle; else state=wash; end
rinse: begin out=0; if(cancel==0 && lid==0 && mode1==1) state=spin; else if(cancel==1)
state=idle; else state=rinse; end
spin: begin out=1; if(cancel==1) state=idle; else state=idle; end
default: state=idle;
endcase
endcase

```

```

end
endmodule

```

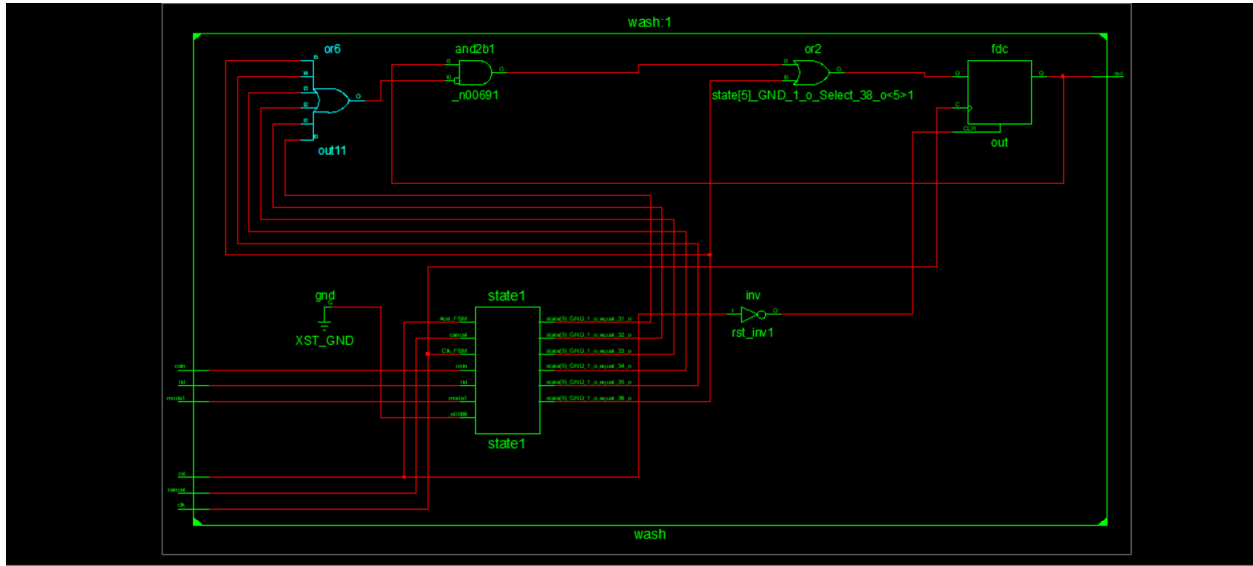

```

module washtest;

    // Inputs
    reg clk;
    reg lid;
    reg coin;
    reg cancel;
    reg mode1;
    reg rst;

    // Outputs
    wire out;

```



```

// Instantiate the Unit Under Test (UUT)
wash uut (
    .out(out),
    .clk(clk),
    .lid(lid),
    .coin(coin),
    .cancel(cancel),
    .mode1(mode1),
    .rst(rst)
);

initial begin
    // Initialize Inputs
    clk = 0;
    lid = 0;
    coin = 0;
    cancel = 0;
    mode1 = 0;
    rst = 0;

    // Wait 100 ns for global reset to finish
    #100;

    clk = 1;
    lid = 0;
    coin = 1;
    cancel = 0;
    mode1 = 0;
    rst = 0;

    #100;

    clk = 1;
    lid = 0;
    coin = 0;
    cancel = 0;
    mode1 = 1;
    rst = 0;

```


```
#100;
```

```
clk = 1;  
  lid = 0;  
  coin = 0;  
  cancel = 0;  
  mode1 = 1;  
  rst = 0;  
  // Add stimulus here  
    #100;  
  clk = 1;  
  lid = 0;  
  coin = 0;  
  cancel = 0;  
  mode1 = 1;  
  rst = 0;  
    #100;
```

```
clk = 1;  
lid = 0;  
coin = 0;  
cancel = 1;  
mode1 = 0;  
rst = 0;
```

```
end
```

```
endmodule
```

 

Trafficlightcontroller

```
module trafficlightcontroller(highway, country, x, clk, reset
);
```

```
input x, clk, reset;
```

```
output reg [1:0]highway, country;
```

```
reg [2:0] state, next_state;
```

```
reg [3:0] count_reg, count_next;
```

```
parameter s0 = 3'b000, s1 = 3'b001, s2 = 3'b010, s3 = 3'b011, s4 = 3'b100;
```

```
parameter red = 2'b00, yellow = 2'b01, green = 2'b10;
```

```
always @ (posedge clk or negedge reset)
```

```
begin
```

```
if (!reset)
```

```
begin
```

```
state <= s0;
```

```
count_reg <= 0;
```

```
end
```

```
else
```

```
begin
```

```
state <= next_state;  
count_reg <= count_next;  
end  
end
```

```
always @ (state, x, count_reg)  
begin  
  case(state)  
    s0 : if (x == 0)  
          next_state <= s0;  
      else  
          begin  
            count_next <= 4'b0011;  
            next_state <= s1;  
          end  
    s1 : if(x == 1)  
          begin  
            count_next <= count_reg - 1'b1;  
            if (count_reg == 4'b0000)  
              begin  
                next_state <= s2;  
                count_next <= 4'b0011;  
              end  
            else next_state <= s1;  
          end  
    s2 : if (x == 1)  
          begin  
            count_next <= count_reg - 1'b1;  
            if (count_reg == 4'b0000)  
              begin  
                next_state <= s3;  
                count_next <= 4'b0011;  
              end  
            else next_state <= s2;  
          end  
    s3 : if (x == 0)  
          next_state <= s4;  
      else next_state <= s3;
```


```

s4 :
  if (x == 0)
    begin
      count_next <= count_reg - 1'b1;
      if (count_reg == 4'b0000)
        begin
          next_state <= s0;
          count_next <= 4'b0011;
        end
      else next_state <= s4;
        end
    default : next_state <= s0;
  endcase
end

always @ (state)
begin
  case (state)
s0 : begin highway <= 2'b10;
      country <= 2'b00;
        end
      s1 : begin highway <= 2'b01;
        country <= 2'b00;
          end
      s2 : begin highway <= 2'b00;
        country <= 2'b00;
          end
      s3 : begin highway <= 2'b00;
        country <= 2'b10;
          end
      s4 : begin highway <= 2'b00;
        country <= 2'b01;
          end
      default : begin highway <= 2'b10;
        country <= 2'b00;
          end
  endcase
end

```

endmodule

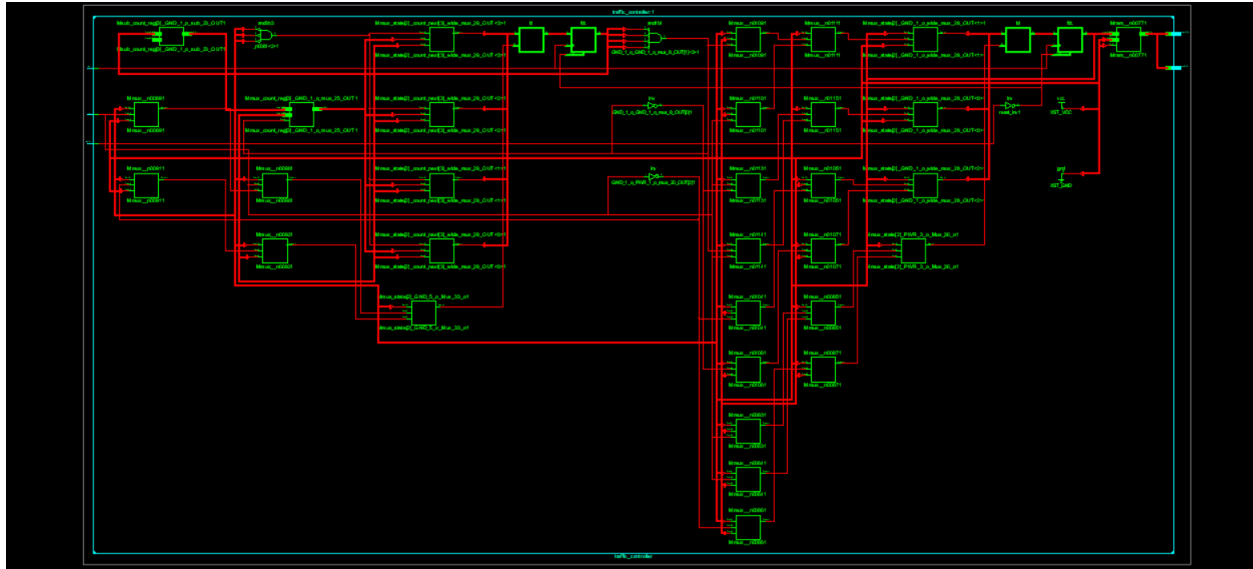

```
module traffictest;
```

```
    // Inputs
    reg x;
    reg clk;
    reg reset;
```

```
    // Outputs
    wire [1:0] highway;
    wire [1:0] country;
```

```
    // Instantiate the Unit Under Test (UUT)
```

```
    traffic_controller uut (
        .highway(highway),
        .country(country),
        .x(x),
        .clk(clk),
        .reset(reset)
```

```
    );
    initial begin
        clk = 1;
```

```

forever #5 clk = ~clk;
end

initial begin
    // Initialize Inputs
    x = 0;

    reset = 0;

    // Wait 100 ns for global reset to finish
    #100;


    reset = 1;
    x = 1;
    #200;
    x = 0;

    // Add stimulus here

end

endmodule

```

 

BUS

```
module bus(r1,r2,r3,resetn,clock,g1,g2,g3
);

    input r1,r2,r3;
    input resetn,clock;
    output reg g1,g2,g3;

    reg[0:1]y,Y;
    parameter Idle=2'b00,gnt1=2'b01,gnt2=2'b10,gnt3=2'b11;

    always@(posedge clock or negedge resetn)
    begin
        if(!resetn)
            y<=Idle;
        else
            y<=Y;
        end

    always@(y,r1,r2,r3)
    begin
        case(y)
        Idle :casex({r1,r2,r3})
            3'b000: Y <= Idle;
            3'b1xx: Y <= gnt1;
            3'b01x: Y <= gnt2;
            3'b001: Y <= gnt3;
            default: Y <= Idle;
        endcase

        gnt1:if(r1)Y <= gnt1;
            else    Y <= Idle;

        gnt2:if(r2)Y <= gnt2;
            else    Y <= Idle;

        gnt3:if(r3)Y <= gnt3;
            else    Y <= Idle;
        default : Y <= Idle;
        endcase
    end
    always@(y)
```




```

begin case(y)
Idle:casex({r1,r2,r3})
    3'b000: begin
        g1<=0;
        g2<=0;
        g3<=0;
    end
    3'b1xx: begin g1 <= 1; g2 <= 0; g3 <= 0; end
    3'b01x: begin g1 <= 0; g2 <= 1; g3 <= 0; end
    3'b001: begin g1 <= 0; g2 <= 0; g3 <= 1; end
    default:begin
        g1<=0;
        g2<=0;
        g3<=0;
    end
endcase
gnt1: if(r1)g1 <= 1;
    else    begin
        g1<=0;
        g2<=0;
        g3<=0;
    end
gnt2: if(r2)g2 <= 1;
    else    begin
        g1<=0;
        g2<=0;
        g3<=0;
    end
gnt3: if(r3)g3 <= 1;
    else    begin
        g1<=0;
        g2<=0;
        g3<=0;
    end
default: begin
    g1<=0;
    g2<=0;
    g3<=0;
end
endcase
end

endmodule

```

 

// Inputs

```
reg r1;
reg r2;
reg r3;
reg resetsn;
reg clock;
```

// Outputs

```
wire g1;
wire g2;
wire g3;
```

// Instantiate the Unit Under Test (UUT)

```
bus_arbiter uut (
    .r1(r1),
    .r2(r2),
    .r3(r3),
    .resetsn(resetsn),
    .clock(clock),
    .g1(g1),
    .g2(g2),
    .g3(g3)
```

```

);
initial begin
    clock = 1;
    forever #5 clock = ~clock;
end

initial begin
    // Initialize Inputs

    resetn = 0;
    #100;
    resetn = 1;
    repeat(5)
    begin
        r1 = $random;
        r2 = $random;
        r3 = $random;
        #100;
    end

    // Wait 100 ns for global reset to finish

    // Add stimulus here

end

endmodule

```

