 


College of Engineering, Pune

Dept. of Electronics and Telecommunication Engineering

Course : **RTL Simulation and Synthesis Lab (FY VLSI & ES)**

Year : 2020-21



RTL Lab 4,5 Report :

Mis : 122035014

Name : Swapnil Hanmant Phalke

1011 sequence detector using moore machine non- overlapping

Code:-

```
module Moore_sequence(X,clk,reset,Y);
input X,clk,reset;
output reg Y;
parameter S0=3'b000,
          S1=3'b001,
          S2=3'b011,
          S3=3'b010,
          S4=3'b110;
reg [2:0] current_state, next_state;
always @(negedge reset,posedge clk)
begin
if(!reset)
current_state <= S0;
else
current_state <= next_state;
end
always @(current_state,X)
begin
case(current_state)
S0:begin
if(X==1'b1)
next_state = S1;
else
next_state = S0;
end
S1:begin
if(X==1'b0)
next_state = S2;
else
next_state = S1;
end
S2:begin
if(X==1'b0)
next_state = S0;
else
```

```
next_state = S3;
end
S3:begin
if(X==1'b0)
next_state = S2;
else
next_state = S4;
end
S4:begin
if(X==1'b0)
next_state = S0;
else
next_state = S1;
end
default:next_state = S0;
endcase
end
always @(current_state)
begin
case(current_state)
S0:Y=0;
S1:Y=0;
S2:Y=0;
S3:Y=0;
S4:Y=1;
default Y=0;
endcase
end
endmodule
```

testbench:

module qw;

```
// Inputs
reg x;
reg clk;
reg rst;
```

```
// Outputs
```

```

        wire y;

        // Instantiate the Unit Under Test
        (UUT)
        mealy uut (
            .x(x),
            .clk(clk),
            .rst(rst),
            .y(y)
        );

        initial begin

            clk = 1;
            forever #60 clk=~clk;
            end

            Inputs
            initial begin// Initialiye

                x = 0;

                rst = 0;

                // Wait 100 ns for global rst
                to finish
                #100;
                // Add stimulus here



            rst=1;
            x = 1;
            #100;
            x=0;
            #100;
            x = 1;
            #100;
            x = 1;
            #100;

            // Add stimulus here

        end

    endmodule

```

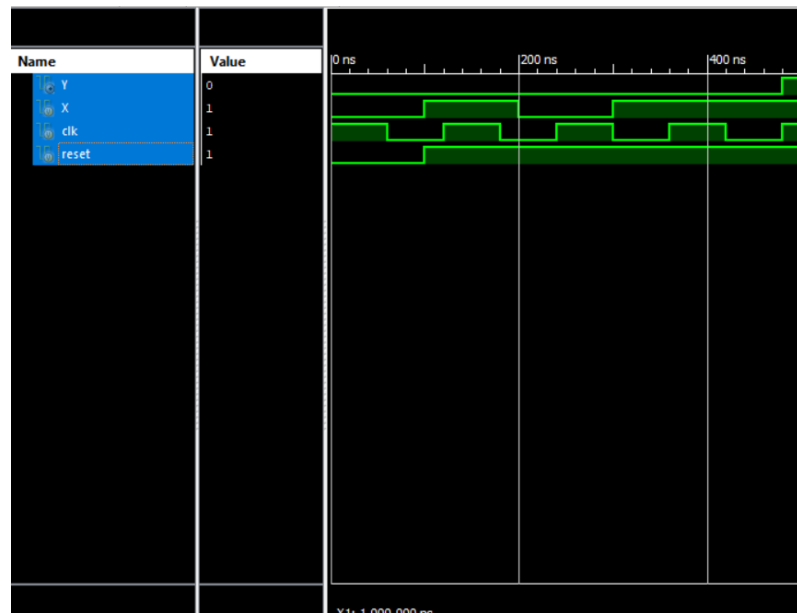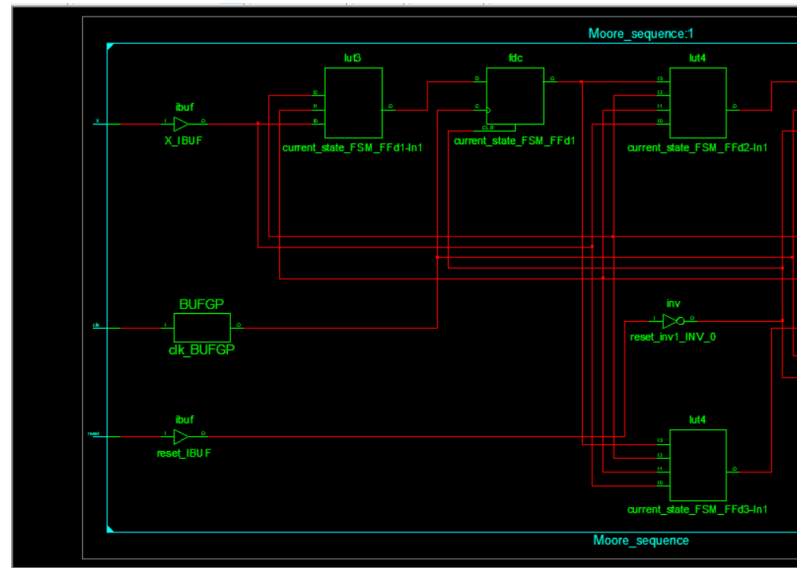

1011 Sequence detector using mealy machine

Code:-

```

module mealy(X,clk,reset,Y);
input X,clk,reset;
output reg Y;
parameter S0=2'b00,
        S1=2'b01,
        S2=2'b10,
        S3=2'b11;
reg [1:0] current_state, next_state;
always @(negedge reset,posedge clk)
begin
    if(!reset)
        current_state <= S0;
    else
        current_state <= next_state;
end
always @(current_state,X)
begin
    case(current_state)
    S0:begin
        if(X==1'b1)
            next_state = S1;
        else
            next_state = S0;
    Y=0;
    end
    S1:begin
        if(X==1'b0)

            next_state = S2;
        else
            next_state = S1;
    Y=0;
    end
    S2:begin

```


```


if(X==1'b0)

    next_state = S0;
    else
        next_state = S3;
Y=0;
end
S3:begin
if(X==1'b0)

    next_state = S2;
    else
        next_state = S0;
Y=1;
end
default:next_state = S0;
endcase
end
endmodule

```

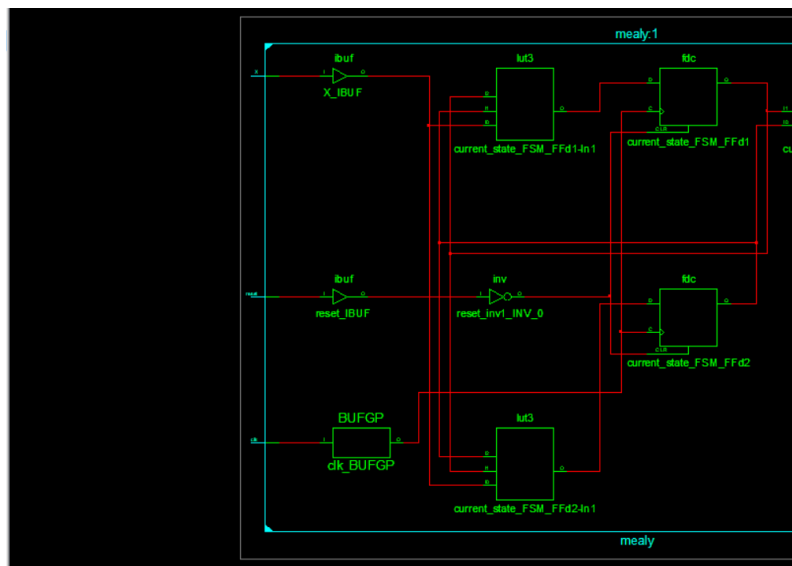

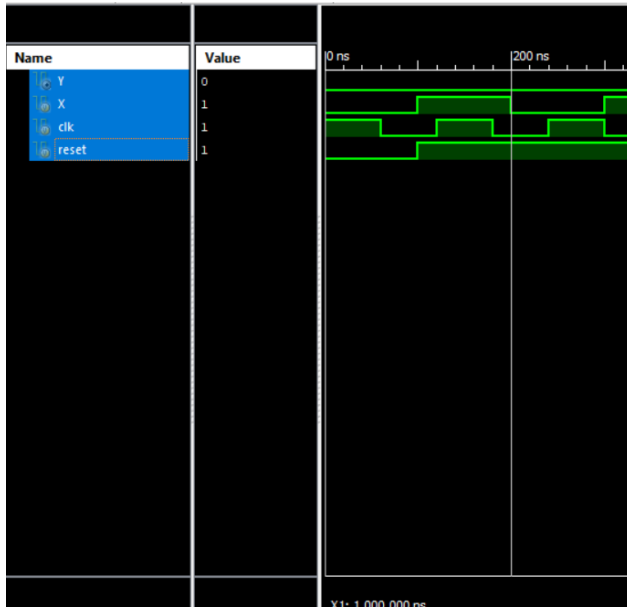

1011 Sequence detector using moore (overlap method)

Code-

```

module Moore_sequence(X,clk,reset,Y);
input X,clk,reset;
output reg Y;
parameter S0=3'b000,
          S1=3'b001,
          S2=3'b011,
          S3=3'b010,
          S4=3'b110;
reg [2:0] current_state, next_state;
always @(negedge reset,posedge clk)
begin
if(!reset)
current_state <= S0;
else
current_state <= next_state;
end
always @(current_state,X)
begin
case(current_state)

```

```

S0:begin
if(X==1'b1)

next_state = S1;
else
next_state = S0;
end
S1:begin
if(X==1'b0)

next_state = S2;
else
next_state = S1;
end
S2:begin
if(X==1'b0)

next_state = S0;
else
next_state = S3;
end
S3:begin
if(X==1'b0)

next_state = S2;
else
next_state = S4;
end
S4:begin
if(X==1'b0)

next_state = S2;
else
next_state = S1;
end
end

```

```

default:next_state = S0;
endcase
end
always @(current_state)
begin
    case(current_state)
        S0:Y=0;

        S1:Y=0;



        S2:Y=0;

        S3:Y=0;

        S4:Y=1;

        default Y=0;
    endcase
end
endmodule

```

 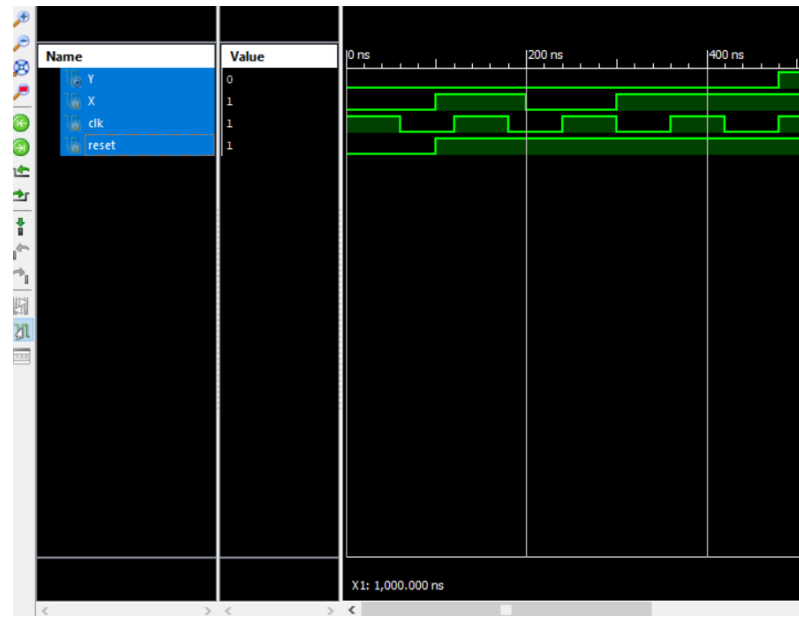

Write a code for Mealy FSM to avoid Glitches

Code:

```
module Mealy(clk,x,z,rst);
input clk,rst,x;
output reg z;
parameter
A=2'b00,B=2'b01,C=2'b11,D=2'b10;
reg [1:0] ps,ns;
always @(posedge clk,negedge rst)
begin
if(!rst)
ps<=A;
else
ps<=ns;
end

always @(ps,x)
begin
case(ps)
A:
if(!x)
begin
ns<=A;
end
else
begin
ns<=B;
end
B:
if(!x)
begin
ns<=C;
end
else
begin
ns<=B;
```

```
end
C:
if(!x)
begin
ns<=A;
end
else
begin
ns<=D;
end
D:
if(!x)
begin
ns<=C;
end
else
begin
ns<=A;
end
default:
ns<=0;
endcase
end

always @(posedge clk ,negedge rst)
begin
if(!rst)
z<=1'b0;
else
begin
z<=1'b0;
case(ps)
A:
if(!x)
z<=0;
else
```



```
z<=0;
B:
if(!x)
z<=0;
else
z<=0;

C:
if(!x)
z<=0;
else
z<=0;

D:
if(!x)
z<=0;
else
z<=1;

endcase
end

end
endmodule
```

 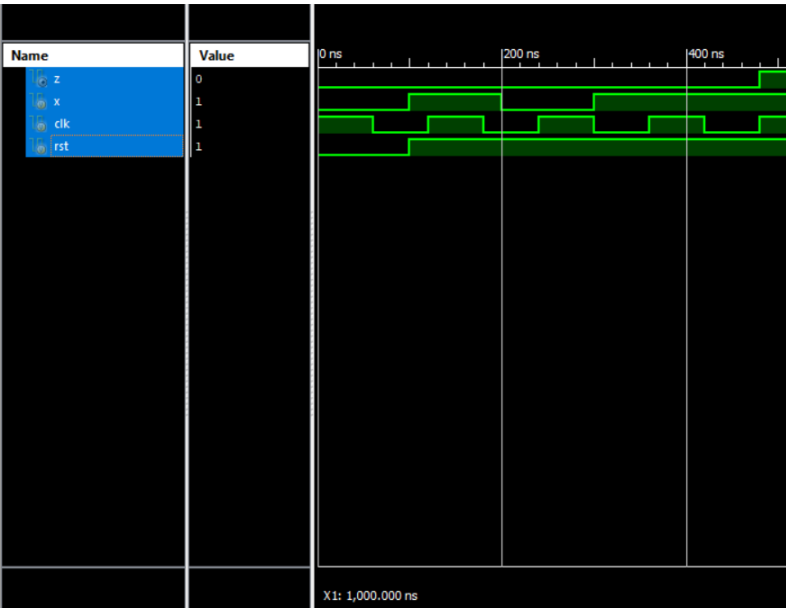

Mealy with one always block

```
module mealy_1alwaysblock(clk,x,z,rst);
input clk,rst,x;
output reg z;
parameter
A=2'b00,B=2'b01,C=2'b11,D=2'b10;
reg [1:0] ps,ns;
always @(posedge clk,negedge rst)
begin
if(!rst)
begin
ps=A;
z=0;
end
else
begin
case(ps)
A: if(!x)
begin
ns=A;
ps=ns;


z=0;
end
else
begin
ns=B;
ps=ns;
z=0;
end
B: if(!x)
begin
ns=C;
ps=ns;

z=0;
end
else
```

```
begin
ns=B;
ps=ns;
z=0;
end
C: if(!x)
begin
ns=A;
ps=ns;

z=0;
end
else
begin
ns=D;
ps=ns;
z=0;
end
D: if(!x)
begin
ns=C;
ps=ns;

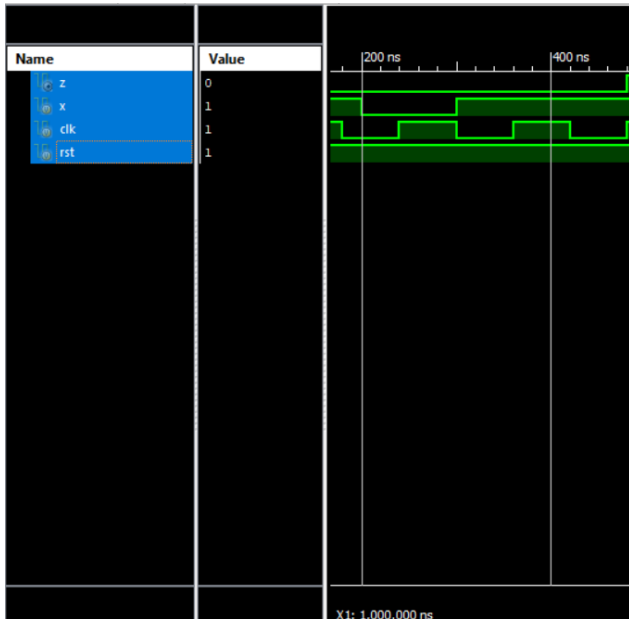z=0;
end
else
begin
ns=A;
ps=ns;
z=1;
end
default:
begin
ns=A;
z=0;
end
endcase
end
```



```
module moore_2alwaysblock(clk,rst,x,y);
input rst,clk,x;
output reg y;
reg [2:0]ps,ns;
parameter s0=3'b000, s1=3'b001 ,s2=3'b010,
```

```
s3=3'b011, s4=3'b100;
always @(posedge clk,negedge rst)
begin
if(!rst)
ps<=s0;
else
ps<=ns;
end
always @(ps,x)
begin
case(ps)
3'b000: begin
y<=1'b0;
if(!x)
ns <=s0;
else
ns<=s1;
end
3'b001: begin
y<=1'b0;
if(!x)
ns <=s2;
else
ns<=s1;
end
3'b010: begin
y<=1'b0;
if(!x)
ns <=s0;
else
ns<=s3;
end
3'b011: begin
y<=1'b0;if(!x)
ns <=s2;
else
ns<=s4;
end
```

```
3'b100: begin
y<=1'b1;
if(!x)
ns <=s0;
else
ns<=s1;
end
default:
begin
y<=1'b0;
ns<=s0;
end
endcase
end
endmodule
```

